



# 3<sup>rd</sup> Romanian Master of Sciences 2010

## Physics – Theoretical Tour

### A. ELECTRICITY

a)  $I_F < 200 \text{ mA}$  (the fuse is intact):

The fuse F acts as a short-circuit, and the voltage across it vanishes. No electric current  $I_1$  flows in  $R_1$ ,  $I_1 = 0$ .

0.25 p

No electric current flows in  $L_2$  for  $t = 0$ , the voltage across the fuse is zero, the electric current  $I_2$  is zero,  $I_2 = 0$ .

0.25 p

Across the inductance  $L_1$  a constant voltage  $V$  causes  $I$  to increase at a constant rate  $V/L_1 = 1000 \text{ A/s}$ .

0.25 p

All electrical current  $I$  flows in the fuse,  $I_F = I$ .

0.25 p

The melting condition is realized for  $t = L_1 I_F / V = 0.2 \text{ ms}$

0.5 p

**total a) 1.5 p**

b) Once the fuse melts, the current  $I_F$  vanishes,  $I_F = 0$ .

0.25 p

Right after the fuse melts, the electric current  $I$  conserves its value before melting,  $I = 200 \text{ mA}$ .

0.25 p

The current flowing in  $L_2$  is free of jumps (discontinuities). Then, right after melting the fuse  $I_2 = 0$ .

0.25 p

As a consequence of Kirchhoff's first law, right after melting the fuse, the current  $I_1$  flowing in  $R_1$  is 200 mA, causing a voltage drop across  $R_1$  of 200 V, with the "+" pole in the right hand side.

0.25 p

As a consequence, a voltage across  $L_1$  develops  $V - R_1 I_F = 200 \text{ V} - 10 \text{ V} = 190 \text{ V}$ , causing the variation of  $I$  at a rate  $\Delta I / \Delta t$

given by  $(V - R_1 I_F) / L_1 = 19000 \text{ A/s}$ . Right after the fuse melts, the voltage polarity causes  $I$  to decrease at the rate above.

0.5 p

The 200 V voltage drop across  $R_1$  produces an increase of  $I_2$ . Right after the fuse melts, the voltage drop across  $R_2$  is zero, therefore, immediately after melting the fuse,  $I_2$  raises at a rate of  $40000 \text{ A/s}$ .

0.25 p

From the first Kirchhoff law, it follows that immediately after the fuse melts, the current  $I_1$  falls at a rate of  $59000 \text{ A/s}$ .

0.5 p

**total b) 2.25 p**

c) For  $t$  approaching infinity:

$I_1 = 10 \text{ mA}$

0.25 p

$I_2 = 50 \text{ mA}$

0.25 p


$I = 60 \text{ mA}$

0.25 p

**total c) 0.75 p**

## B. MICHELSON'S "LADDER"

a. 1.5p

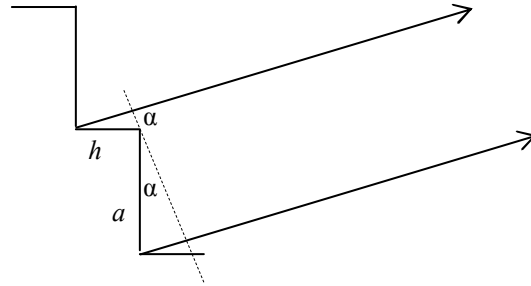

It is obvious that for  $\alpha = 0$ , the path length difference  $\delta$  between two neighboring light rays is  $(n - 1)h$ . This difference increases with  $\alpha$ .

$$\delta = nh + a \sin \alpha - h \cos \alpha = (n - 1)h + a \sin \alpha + h(1 - \cos \alpha) .$$

$$\delta = k\lambda , k \in \mathbb{N} .$$

One can see that in our specific example we get a diffraction maximum for  $\alpha = 0$  and  $k_0 = 10,000$ . So the condition for the principal maxima can be written:

$$a \sin \alpha + h(1 - \cos \alpha) = p\lambda , p = k - k_0 > 0 .$$

b. 1.5p

One knows that the intensity of the light diffracted by a slit with aperture  $a$  depends on the deflecting angle according to:

$$I(\alpha) = I_0 \left[ \frac{\sin \left( \frac{\pi a \sin \alpha}{\lambda} \right)}{\frac{\pi a \sin \alpha}{\lambda}} \right]^2 .$$

The first diffraction minimum occurs for

$$\frac{\pi a \sin \alpha}{\lambda} = \pi \Rightarrow \sin \alpha = \frac{\lambda}{a} = 5 \cdot 10^{-5} .$$

For such a small angle,

$$\delta \approx a\alpha + h \frac{\alpha^2}{2} \approx a\alpha \approx a \sin \alpha = p\lambda .$$

$$\sin \alpha < \frac{\lambda}{a} \Rightarrow p < 1 \Rightarrow p = 0 \Rightarrow k = k_0 .$$

So the only principal maximum that can be seen is the "central" one.

c. 1.5p

Increasing the wavelength of the light stream by  $\Delta\lambda$  can lead to the overlapping of two such central maxima.

$$k_0\lambda = (k_0 - 1)(\lambda + \Delta\lambda) \Rightarrow \Delta\lambda \approx \frac{\lambda}{k_0} = 0.5\text{A} .$$